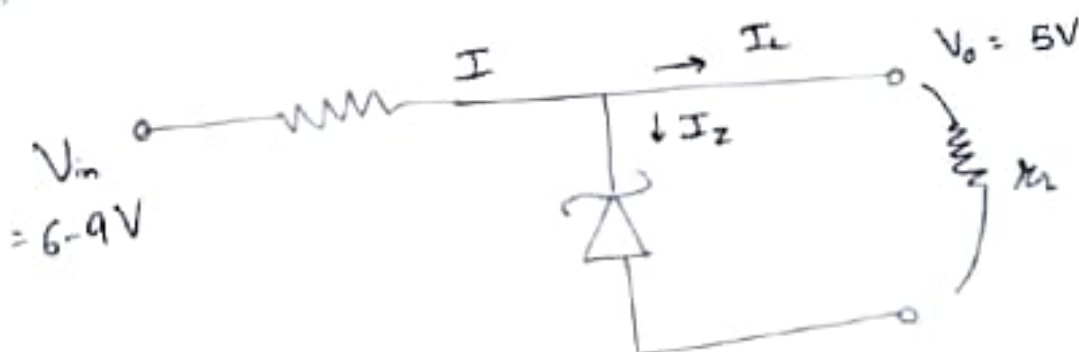


Q1.



For a 5V output, with 2A load current & 0.01 A Zener current, we have $I = 2.01$ A. (1)

This will lead to the value of $R_s = \frac{V_{in} - V_o}{I}$

$$= \frac{6-5}{2.01}$$

We take low value of V_{in} to find the highest R_s that can work for us.

Now, for power ratings, worst case is $V_{in} = 9V$

$$P_s = \frac{(V_{in} - V_z)^2}{R_s}$$

$$= \frac{16}{0.497} = 32.16 \text{ W} \quad (2)$$


Worst case for Zener power is when $I_L = 0$.

$$\begin{aligned} P_z &= I_z V_z \\ &= I V_z \\ &= \left(\frac{V_{in} - V_z}{R_s} \right) V_z \end{aligned}$$

$$P_z = 40.2 \text{ W} \quad (3)$$

Q2. For $x=0$, $C_0 = C_1 + C_2$

The equivalent circuit is:

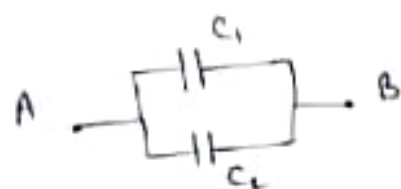

$$C_0 = \frac{\epsilon A}{d} + \frac{\epsilon A}{d} = \boxed{\frac{2\epsilon A}{d}} \quad (2)$$


For any value of x :

$$C_1 = \frac{\epsilon A}{d-x} \quad \& \quad C_2 = \frac{\epsilon A}{d+x}$$


$$C = \epsilon A \left[\frac{1}{d-x} + \frac{1}{d+x} \right]$$

$$C = \boxed{\frac{2d\epsilon A}{d^2 - x^2}} \quad (4)$$
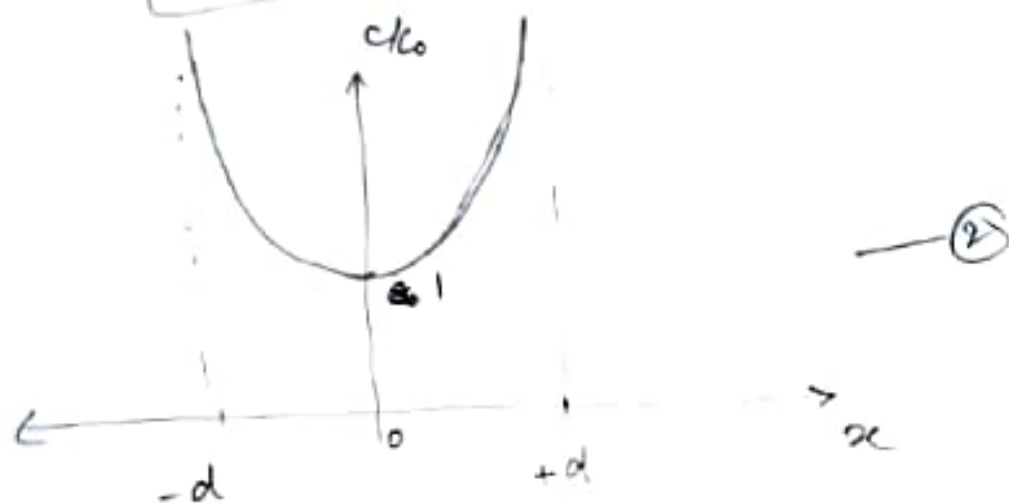
$$\boxed{\frac{C}{C_0} = \frac{d^2}{d^2 - x^2}} \quad (2)$$




Q. To calculate R_{th}

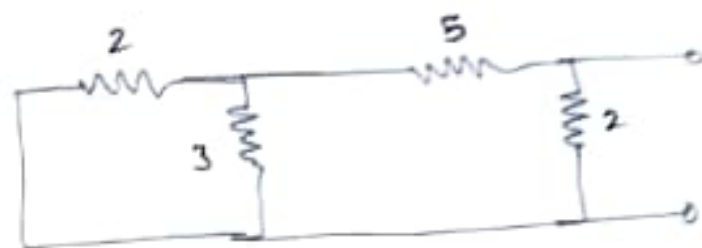

$$R_{th} = 2 \parallel (5 + (2 \parallel 3))$$

$$= 2 \parallel (31/5)$$
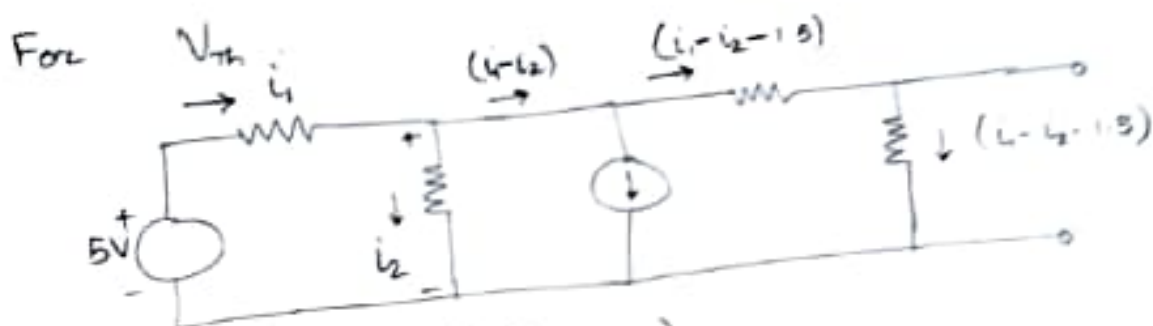
$$= 62/41 = \boxed{1.51 \Omega} \quad (4)$$



$$V_{th} = 2(i_1 - i_2 - 1.5)$$

We have: $2i_1 + 3i_2 = 5$

$$-3i_2 + 7(i_1 - i_2 - 1.5) = 0$$

$$\therefore -10i_2 + 7i_1 = 10.5$$

Then


$$20i_1 + 21i_1 = 50 + 31.5$$

$$i_1 = 81.5/41 \text{ A}$$

$$i_2 = 42/41 \text{ A}$$


$$\boxed{V_{th} = -22/41 \text{ V}} \quad (4)$$

Equivalent
Diagram

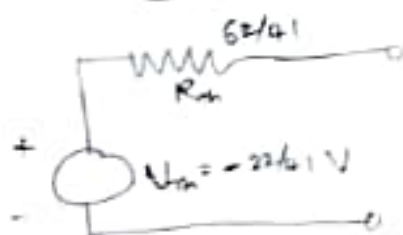


(2)


Q4

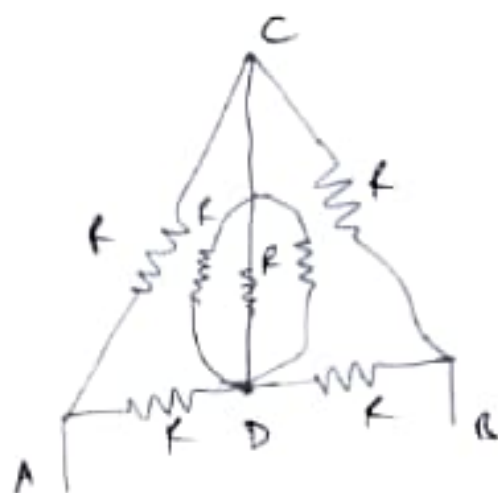

Equivalent circuit

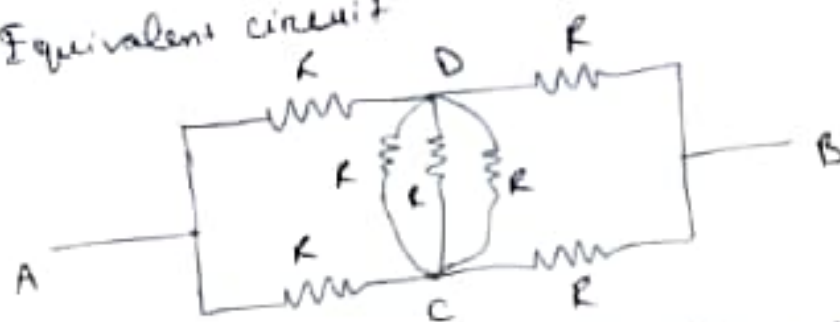

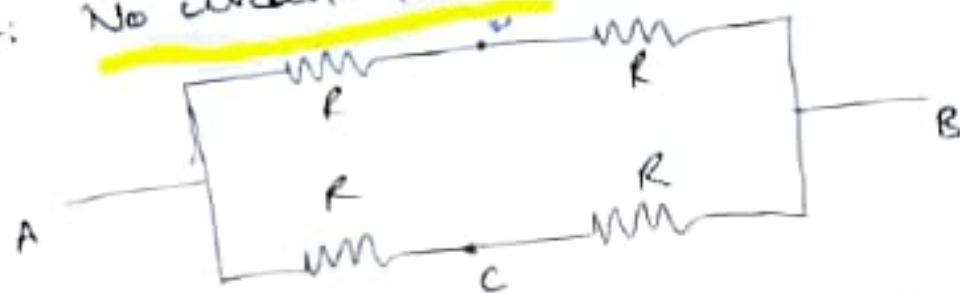This is a balanced Wheatstone bridge
 \therefore No current through the CD branch



Equivalent resistance $2R \parallel 2R$

$$= R$$