

Lecture 6 – Thevenin Theorem

Dr. Aftab M. Hussain,
Associate Professor, PATRIOT Lab, CVEST

The Thevenin Theorem

- Named after Léon Charles Thévenin, a French engineer working in telegraphy who published the theorem in 1883
- The theorem, at that time, was an interesting new way of simplifying electronic circuits
- A note with English translation of the full text, was published as: "[*On a New Theorem in Dynamic Electricity*](#)", *The Telegraphic Journal and Electrical Review*. **XIV** (819). London: H. Alabaster, Gatehouse & Co.: 11 5 January 1884
- One source states that the theorem was "originally enunciated by Helmholtz and should more correctly be called Helmholtz's theorem."

"Extension de la loi d'Ohm aux circuits électromoteurs complexes" [Extension of Ohm's law to complex electromotive circuits], *Annales Télégraphiques* (Troisième série), vol. 10, pages 222–224.



The Theorem

- *Given a system of connected linear conductors, including the electromotive forces $\mathcal{E}_1, \mathcal{E}_2, \dots, \mathcal{E}_n$ randomly distributed, consider two points \mathcal{A} and \mathcal{A}' belonging to the system and having potentials \mathcal{V} and \mathcal{V}' .*
- *If points \mathcal{A} and \mathcal{A}' are joined by a wire $\mathcal{A}\mathcal{B}\mathcal{A}'$ of resistance r containing no electromotive force, the potentials of points \mathcal{A} and \mathcal{A}' are changed from \mathcal{V} and \mathcal{V}' , but the current i which flows in the wire is given by the formula:*

$$i = \frac{V - V'}{r + R}$$

- *Where \mathcal{R} is the resistance of the original system, measured between the points \mathcal{A} and \mathcal{A}' considered the electrodes.*
- In modern parlance, we call $V - V' = V_{oc}$ and $R = R_{th}$

The Theorem

- *Thus Ohm's formula is applicable not only to simple circuits containing sources with well-defined poles such as a battery or generator, but also to any network of conductors, which can then be considered as generators with arbitrary poles, and having an electromotive force, in each case, equal to the difference of potential previously existing at the two points chosen as poles.*
- *This rule, which doesn't seem to have previously appeared in the journal, is very useful in certain theoretical calculations. From a practical point of view, it permits immediate calculation, given two values which are easily determined experimentally, the value of current which will flow through a branch added to a network of conductors, without the necessity of dealing with the internal components of the network.*

The Proof

- *To demonstrate the theorem, suppose one introduces in the wire ABA' an electromotive force $-E$, equal and opposite to the potential difference $V - V'$. No current will flow in conductor ABA' . Therefore, the system of electromotive forces $-E, E_1, E_2, \dots, E_n$, causes a distribution of currents, among which the one in conductor ABA' is zero.*
- *Suppose now that, in the same conductor, one introduces, joined to the first, a second electromotive force $+E$, equal to the potential difference $V - V'$, and of the same polarity. The force $+E$ causes a new current distribution, which is simply superimposed on the previous one. Among these new currents, that which flows in conductor ABA' is precisely the current i , since the effects of the forces $+E$ and $-E$, equal and opposite, cancel one another. The current i being due only to the force $+E = V - V'$, in the branch r , one is able, by calling R a certain resistance, to write, that according to Ohm's formula,*

$$i = \frac{V - V'}{r + R}$$


The Proof

- *Moreover, the significance of the quantity \mathcal{R} is immediately apparent; it is the resistance of a wire which may replace the original network of conductors between \mathcal{A} and \mathcal{A}' , so that the proper output of a constant source of electric current in branch \mathbf{r} is not changed. The quantity \mathcal{R} now has a precise physical meaning, and it can be called the resistance of the original network measured between the points \mathcal{A} and \mathcal{A}' considered as electrodes. The statement of the theorem follows immediately from this definition.*
- This theorem, only 1 page long, is one of the most important in electronics history.
- Unfortunately, did not receive the level of attention it deserved, neither did Thevenin


The Algorithm

1. Determine the circuit to be converted and identify its two terminals
 2. Keep the terminals open circuit and calculate the voltage across it (call it V_{oc})
 3. Make the circuit inactive by replacing the sources in the circuit:
 1. Short circuit for a voltage source
 2. Open circuit for a current source
 4. Calculate the resistance across the terminal for this configuration (call it R_{th})
 5. Connect V_{oc} and R_{th} in series with the two terminals. This is the equivalent circuit for the circuit under consideration
- Note: We can also short the terminals and calculate the current through it (call it I_{sc}). It will be seen that $V_{oc} = R_{th}I_{sc}$

Examples

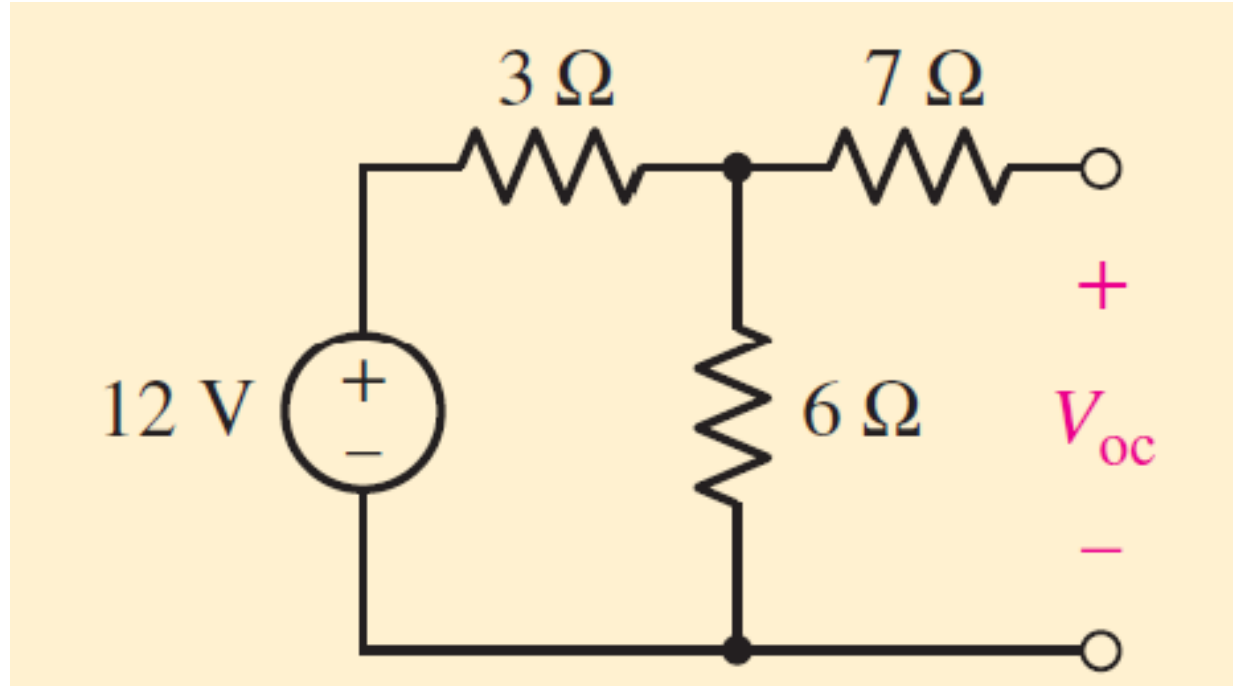


Examples

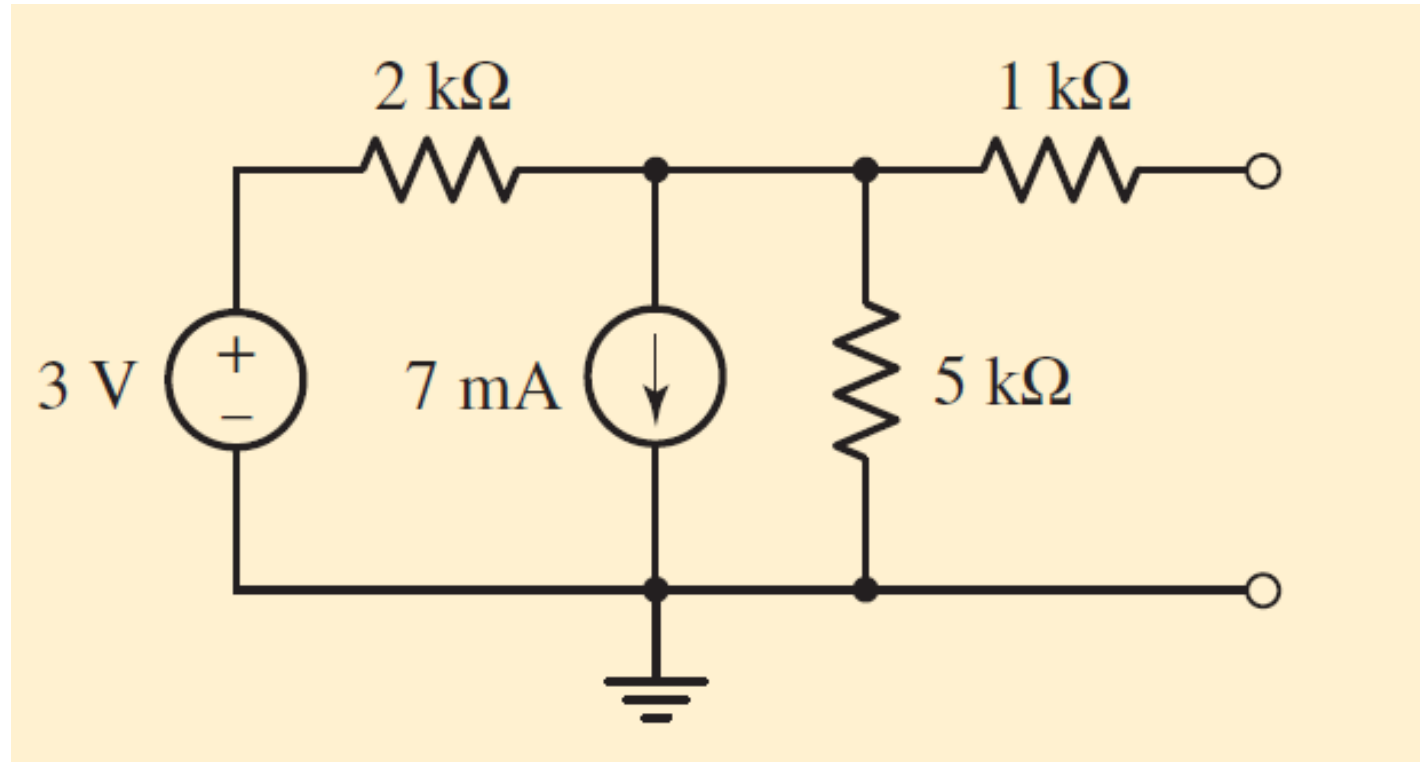

$$V = -7.857 \text{ V}; R = 2.429 \text{ k}\Omega$$

Examples

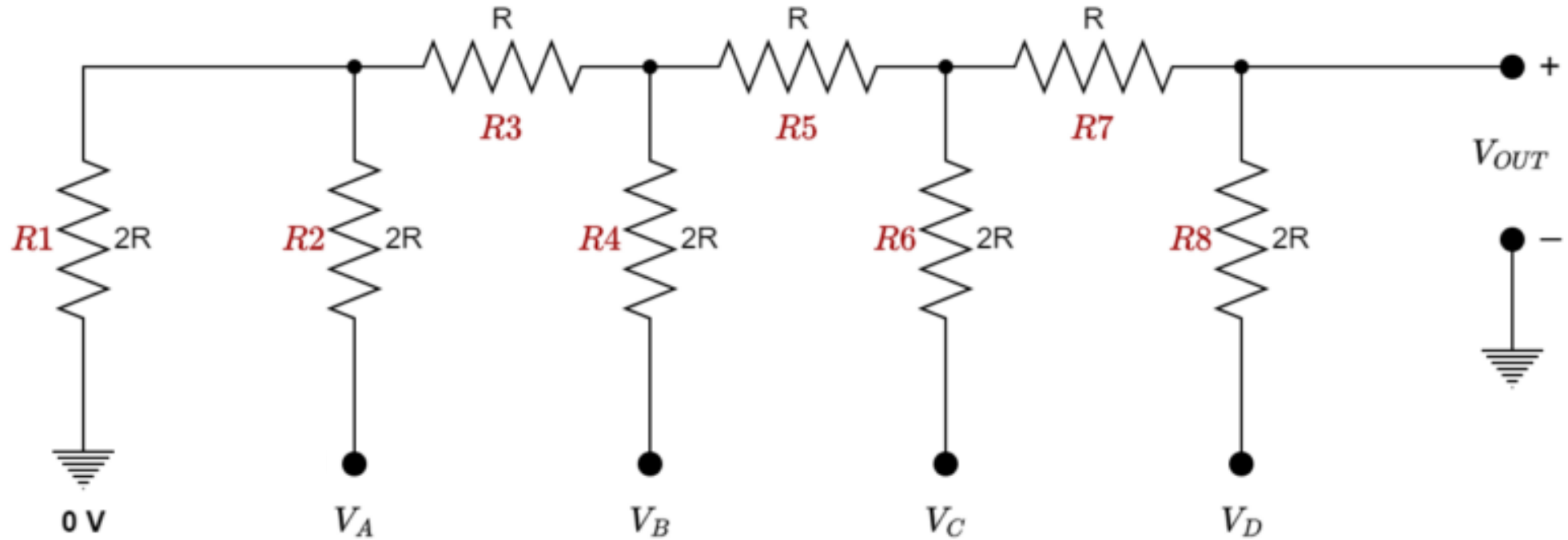

This is the famous R-2R ladder. More about this in CCIoT course, UG2!