

LAB REPORT 1

Introduction to DSO, Breadboard and RC Circuit

Sricharan Vinoth Kumar (2024112022), Saikiran S (2024112007)

M24EC2.102: Electronics Workshop-1

Team ID: 23

Due: 29th September 2024

Objective:

To measure the actual time constant of a given RC circuit using a Digital Storage Oscilloscope.

Equipment Needed:

- Breadboard
- Resistors (Various values)
- Capacitors (Various values)
- Digital Storage Oscilloscope (DSO)

Procedure:


1. Connect the RC circuit on the breadboard as shown in the Circuit Diagram given below.
2. Apply a square wave using the wave generator option in the DSO.
3. Observe the waveform across the capacitor on the DSO screen.
4. For each combination of R and C:
 - a. Calculate the theoretical time constant (τ) using: $\tau = R * C$
 - b. Measure the practical time constant from the DSO waveform and the cursors tool.
 - c. Calculate the theoretical cutoff frequency (f_c) using: $f_c = 1 / (2\pi * R * C)$
5. Record your results in an observation table.
6. Repeat steps 4-5 for three different combinations of R and C values.

Observation and Circuit Diagram:

Observation Table

S.No.	R (in Ohms)	C (in μF)	Time Constant (Theoretical)	Time Constant (Practical)	Cutoff Frequency (Theoretical)
1.	380 Ω	0.01 μF (103)	$3.8 \times 10^{-6} s$	4.3 μs	41.88
2.	4.65 K Ω	0.1 μF (104)	$4.65 \times 10^{-4} s$	3.72 μs	342.3
3.	10 K Ω	0.01 μF (102)	$10 \times 10^{-6} s$	1 μs	2814

Circuit diagram

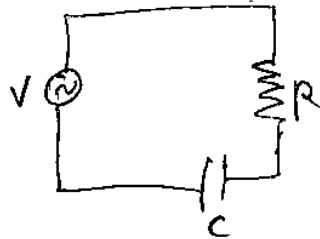

Devans

Calculations:

- For first combination of R and C:

$$\tau = R * C$$

$$\tau = (380 \Omega) * (0.01 \mu F)$$

$$\tau = 3.80 \mu s$$

- For second combination of R and C:

$$\tau = R * C$$

$$\tau = (4.65 \text{ K}\Omega) * (0.1\mu\text{F})$$

$$\tau = 465 \mu\text{s}$$

- For third combination of R and C:



$$\tau = R * C$$

$$\tau = (1 \text{ K}\Omega) * (0.01\mu\text{F})$$



$$\tau = 465 \mu\text{s}$$

Images of Experiment Performed:




- For the First Pair of R and C values:

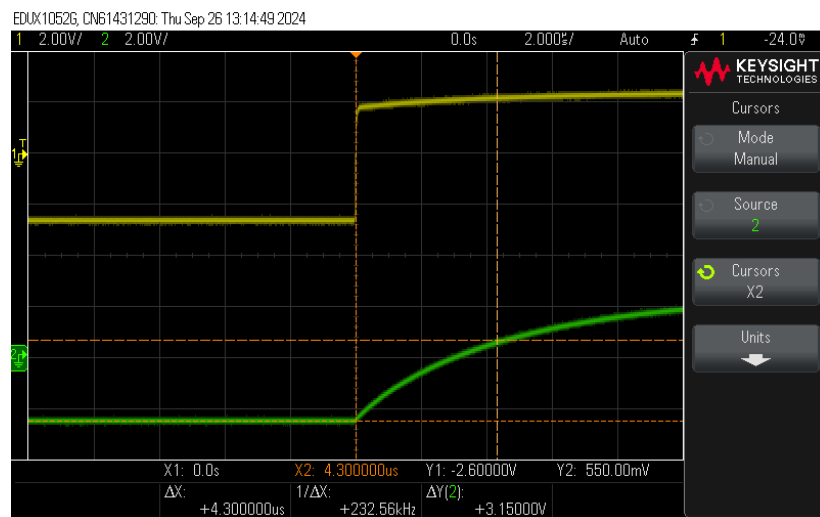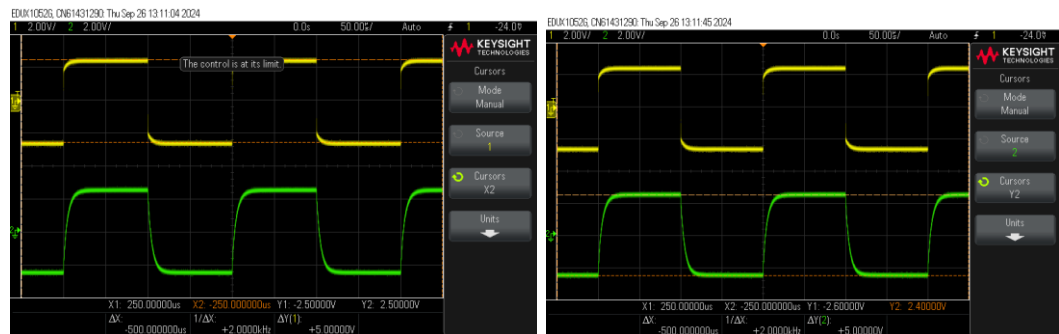

- For the second Pair of R and C values:

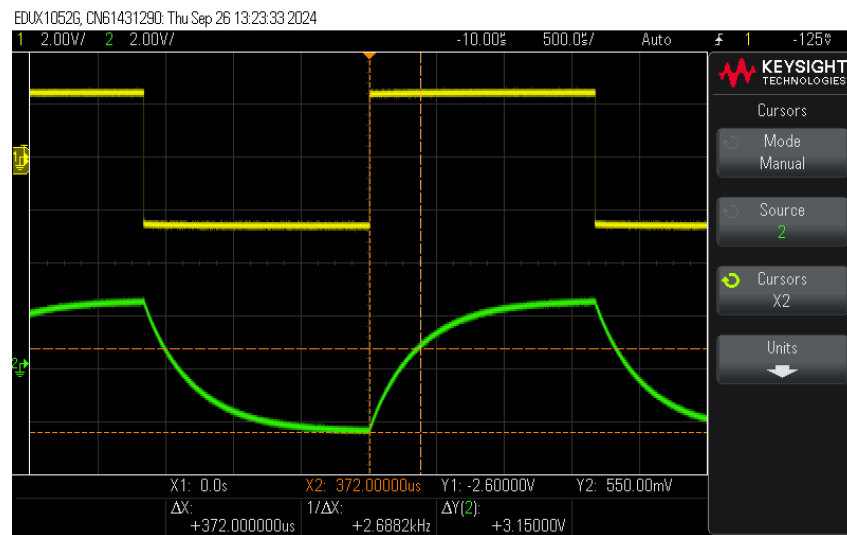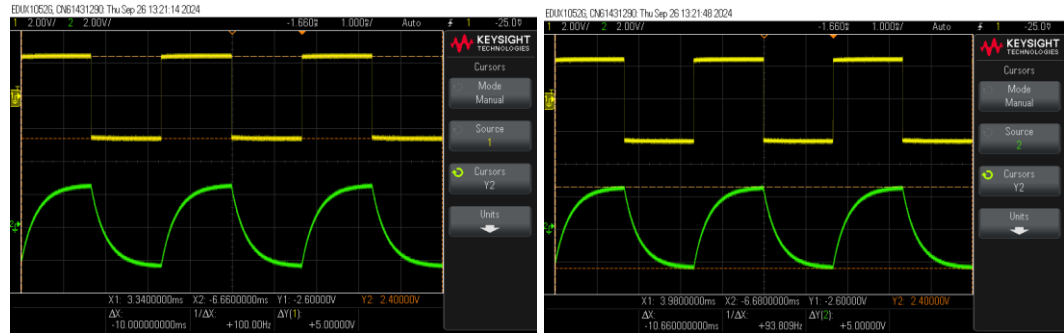

- For the third Pair of R and C values:

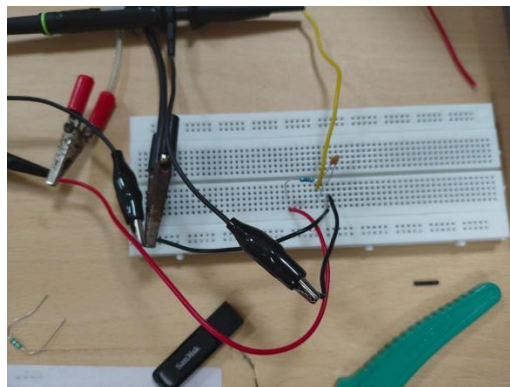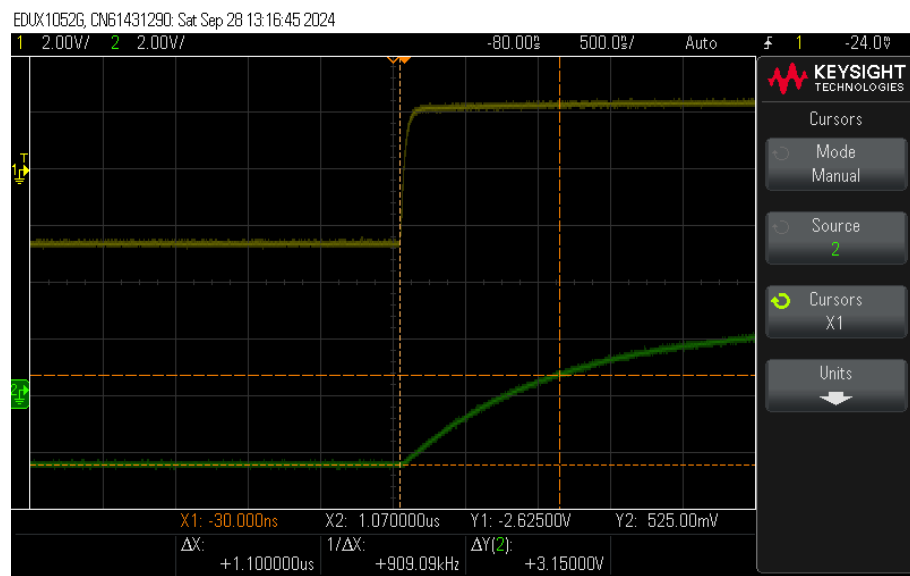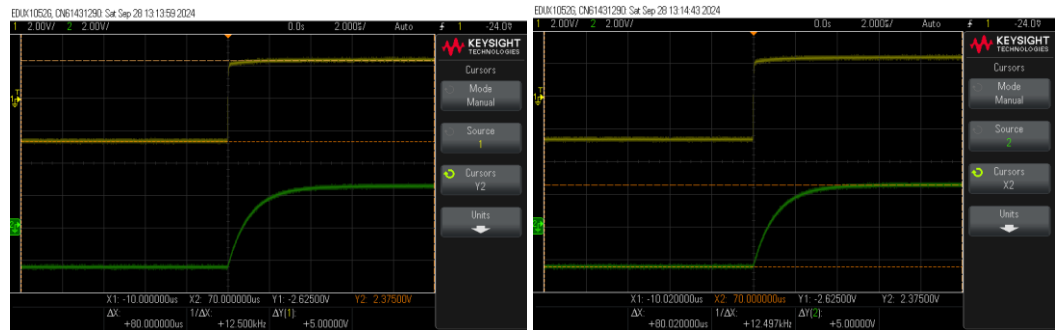

An RC circuit Implemented on the breadboard

Sources of Error:

- Resistor Tolerance: Resistors can have a slightly different value based on their Tolerance.
- Breadboard connections: Connections might be loose which might induce an error in the actual value of time constant.
- Precision of Cursor tool: Using cursors to measure the time constant introduces some human error due to their limited precision.

Conclusion:

Thus the time constants for different RC circuits have been verified experimentally.