

# Lecture 9 – The Inductor

Dr. Aftab M. Hussain,  
Associate Professor, PATRIOT Lab, CVEST

# Q1


---

Q1. Say we are tasked with designing a 5V, 2A regulated power supply. We chose the Zener diode circuit to do this, with an input power supply that can go from 6 to 9 V. Assume the Zener chosen has a 10 mA minimum current for the Zener effect. What should be the specifications for the Zener and the series resistor?

[10 marks]

## Q2

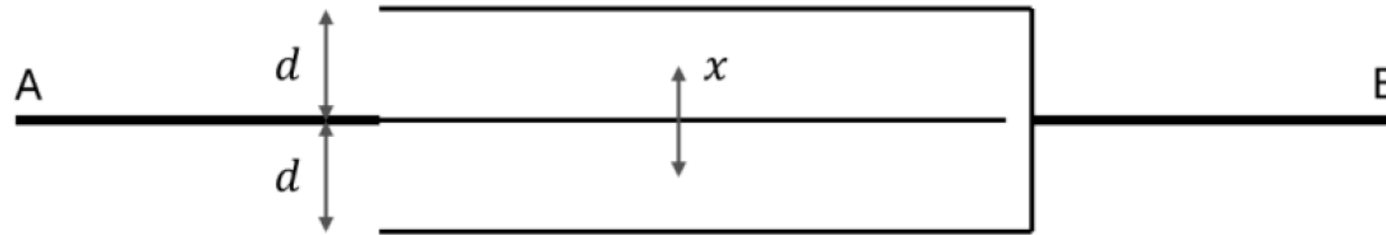
Q2. Accelerometers are made using a capacitive structure with a movable plate. Refer to the structure shown in the figure. Initially the plate is in the middle ( $x = 0$ ). If the middle plate moves vertically by  $x$ , what is the equivalent capacitance of the system with respect to the initial capacitance of the system ( $C_0$ )? Make a rough plot of  $C/C_0$  with  $x$ . Assume plate area is the same in all cases. Ignore fringe capacitance effects. Assume  $x < d \ll \text{linear dimensions}$ .



[10 marks]

# Q3

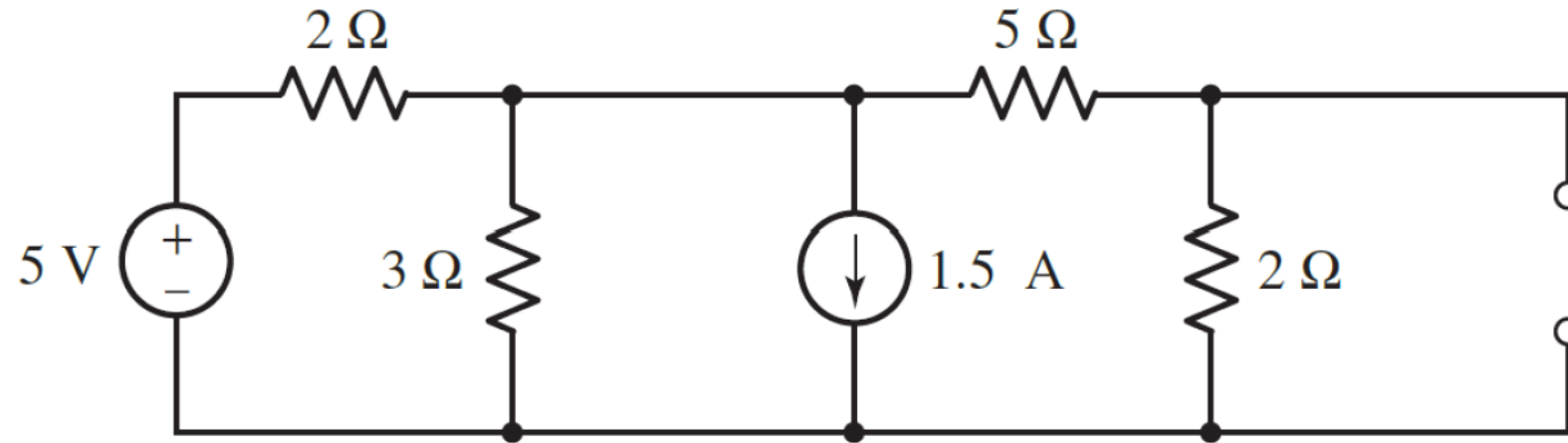
Q3. Create the Thevenin equivalent circuit for the circuit given below:



[10 marks]

# Q4

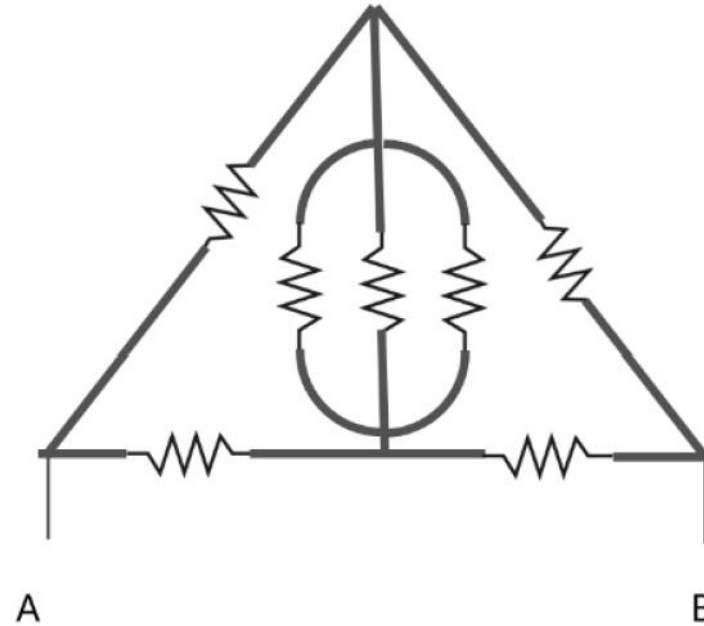Q4. Find the equivalent resistance of the Deathly Hallows symbol, between A and B. All resistors are  $R$ .



[10 marks]

# Current and magnetic field

- Experiments involving currents and magnetic field are very old
- Danish scientist Hans Christian Ørsted showed that a current-carrying conductor produced a magnetic field (i.e. compass needles were affected in the presence of a wire when current was flowing)
- Shortly thereafter, Ampère (in competition with Biot-Savart) made some careful measurements which demonstrated that this magnetic field was *linearly* related to the current which produced it

$$B \propto i$$



Hans Christian Ørsted




André-Marie Ampère

# Electromagnetic induction

- Some years later, the inverse effect was discovered – that magnetic fields can also produce currents
- In this case, the magnetic fields had to be changing, and the voltage induced because of them was proportional to the rate of change of the field

$$v \propto \frac{dB}{dt}$$

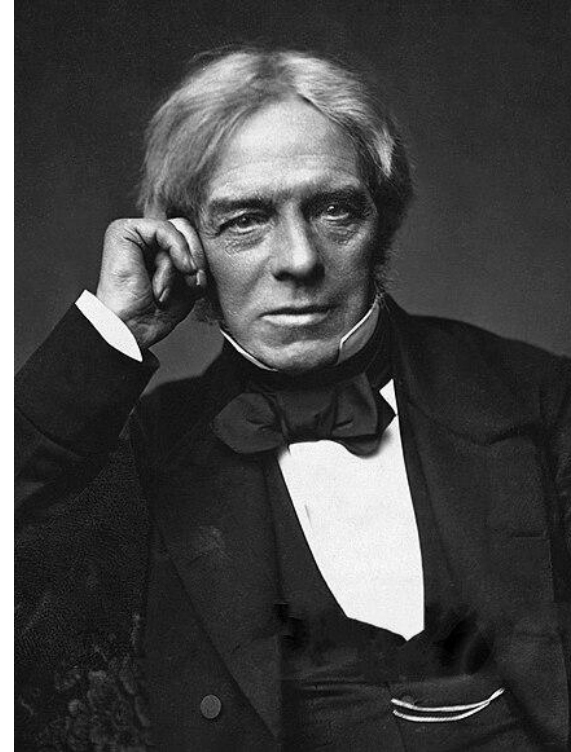- Discovered by Micheal Faraday (in competition with Joseph Henry)



Michael Faraday





Joseph Henry



# Self induction

- As it turns out, a voltage is induced in the wire carrying the current itself, ie, a change in the current of a wire causes a change in the magnetic field around it
- This change in the magnetic field causes a voltage to be induced in the wire itself
- This is self inductance, and the coefficient of proportionality is the inductance of a wire

$$v = L \frac{di}{dt}$$

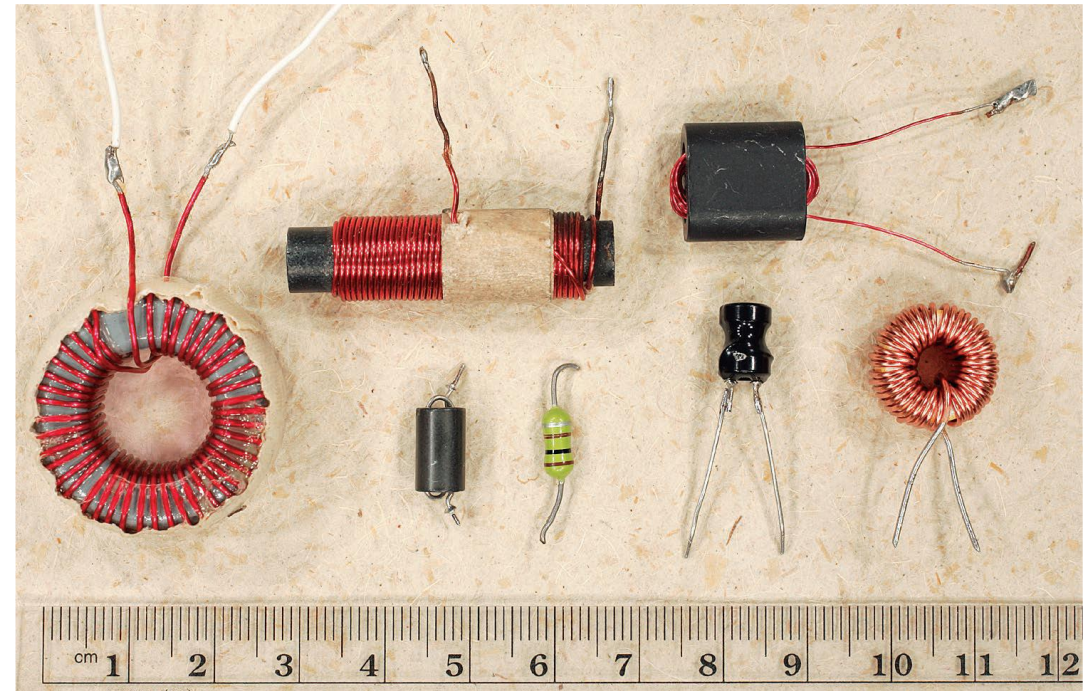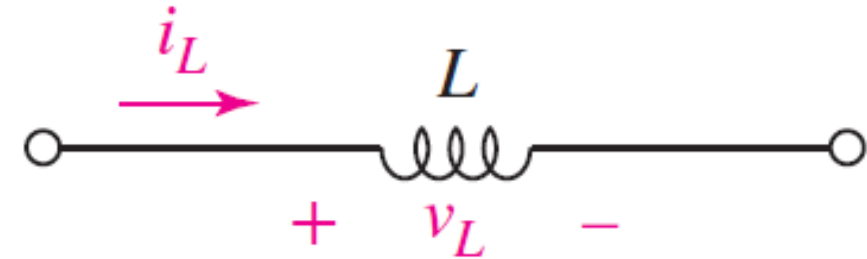




# Energy storage

- For an increasing current  $i(t)$ , there is a voltage induced  $v(t)$  that is opposing the change
- Thus, the current needs to exert “work” to increase
- This work is stored as potential energy in the coil

$$p(t) = i(t)v(t)$$

$$p = iL \frac{di}{dt}$$
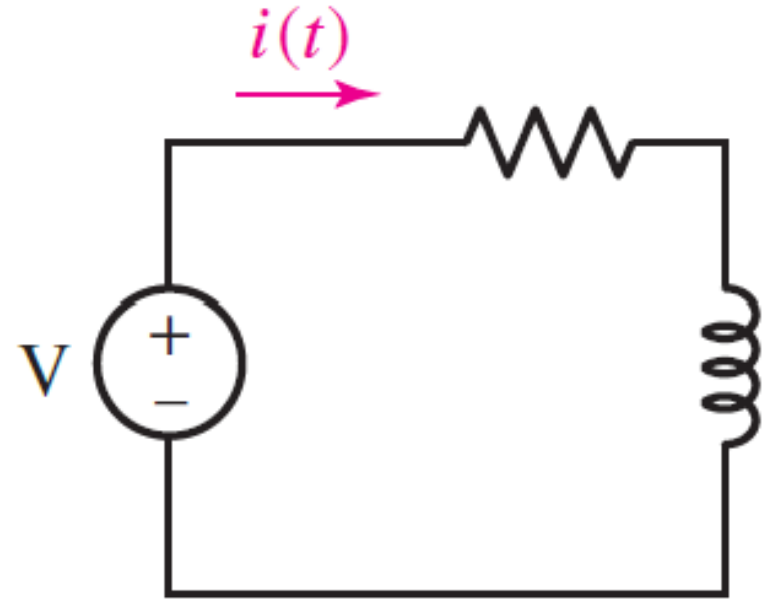
$$E = \int p \, dt = L \int_0^I i \, di = \frac{1}{2} LI^2$$



# Inductors in series

- From KVL:

$$v_s = v_1 + v_2 + \cdots + v_n$$
$$v_s = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \cdots + L_n \frac{di}{dt}$$



$$v_s = (L_1 + L_2 + \cdots + L_n) \frac{di}{dt}$$

- For the equivalent circuit:

$$v_s = L_{eq} \frac{di}{dt}$$

- Thus,

$$L_{eq} = L_1 + L_2 + \cdots + L_n$$

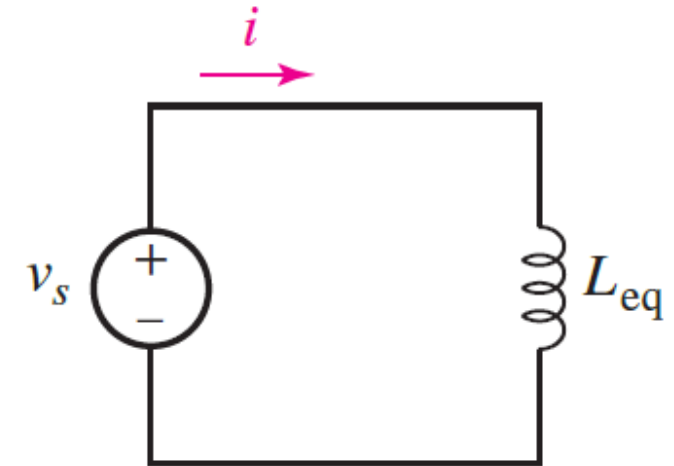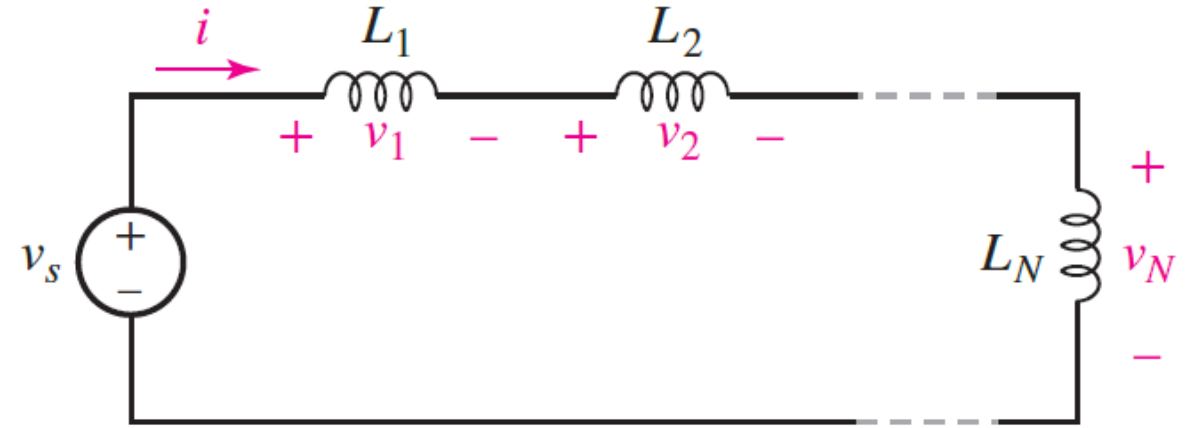

# Inductors in parallel

- From KCL:  $i_s = i_1 + i_2 + \dots + i_n$

$$v = L_i \frac{di_i}{dt}$$

$$i_i = \frac{1}{L_i} \int v dt$$

$$i_s = \frac{1}{L_1} \int v dt + \frac{1}{L_2} \int v dt + \dots + \frac{1}{L_n} \int v dt$$


$$i_s = \left( \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right) \int v dt$$

- For the equivalent:


$$i_s = \frac{1}{L_{eq}} \int v dt$$

- Thus,
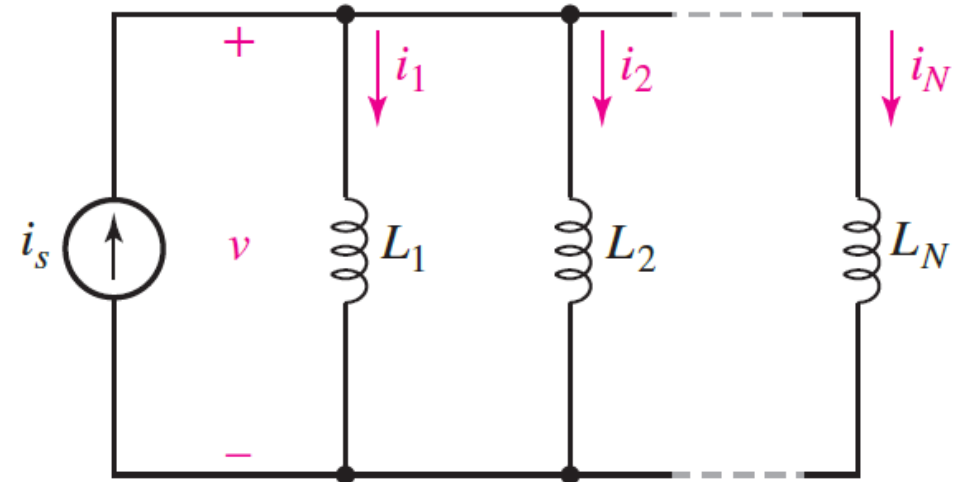
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$



(a)

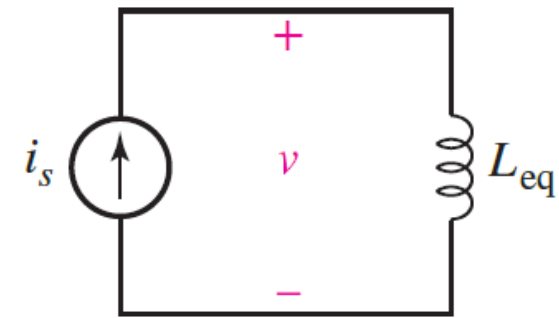


(b)

# RL circuit

- When we connect an inductor to the a voltage source through a resistor, the current in the circuit wants to rise immediately, ie, from zero to  $V/R$
- However, the inductor does not allow that to happen, creating a back EMF of  $di/dt$
- At any given time, the KVL can be written:

$$V = iR + v_L$$
$$V = iR + L \frac{di}{dt}$$
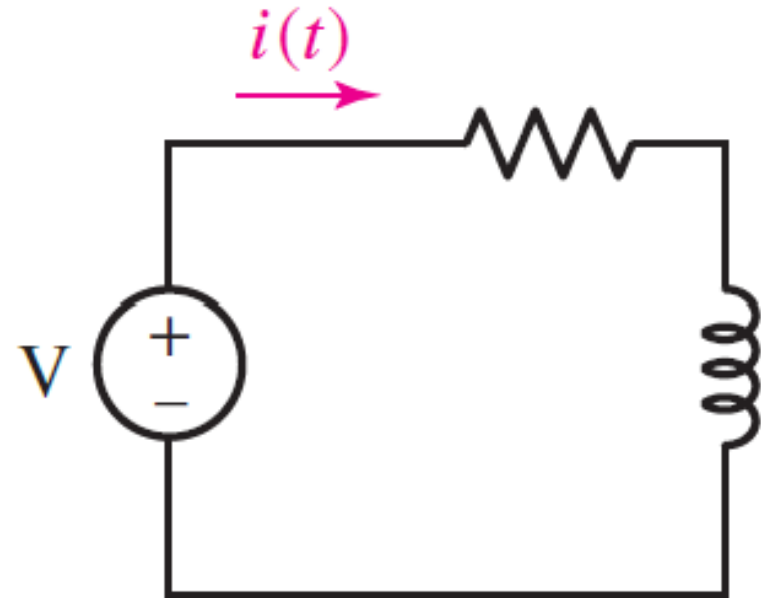
$$\frac{di}{(V - iR)} = \frac{dt}{\frac{L}{R}}$$
$$-\ln(V - iR) = \frac{Rt}{L} + A$$



# RL circuit

$$-\ln(V - iR) = \frac{Rt}{L} + A$$

At  $t = 0, i = 0$

Thus,

$$\ln\left(\frac{V}{V - iR}\right) = \frac{Rt}{L}$$
$$V - iR = Ve^{-\frac{Rt}{L}}$$
$$i = \frac{V}{R} \left(1 - e^{-\frac{Rt}{L}}\right)$$

Thus, at  $t = 0$ , the current is zero. It gradually increases to  $V/R$  as  $t \rightarrow \infty$

$$v_L = L \frac{di}{dt} = Ve^{-\frac{Rt}{L}}$$

