

Lecture 5 – Equivalent circuits

Dr. Aftab M. Hussain,
Associate Professor, PATRIOT Lab, CVEST

Equivalent circuits

- Many times, we replace a part of an electronic circuit with an equivalent
- The idea is to simplify the analysis of the behaviour of the rest of the system
- To qualify as an “equivalent”, a circuit should have the following properties:
 - Same number of terminals as the original
 - Same current at all nodes and same voltage across all terminals, as the original circuit
 - Same behaviour when an external condition is changed

Resistance networks



- The simplest example of equivalent circuits is resistive networks
- We know that, for resistances in series:

$$R_{eq} = \sum R_i$$


- For parallel resistors:

$$\frac{1}{R_{eq}} = \sum \frac{1}{R_i}$$


- In the case when the resistive network is more complex, we can apply this technique multiple times to get an equivalent

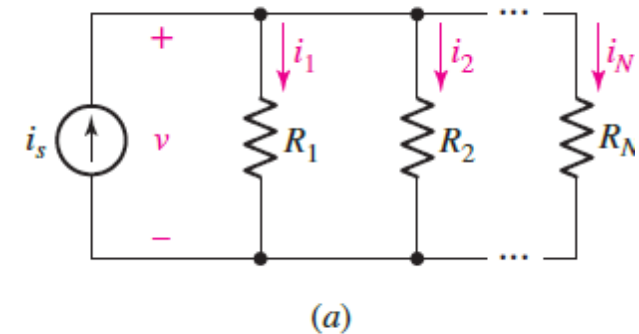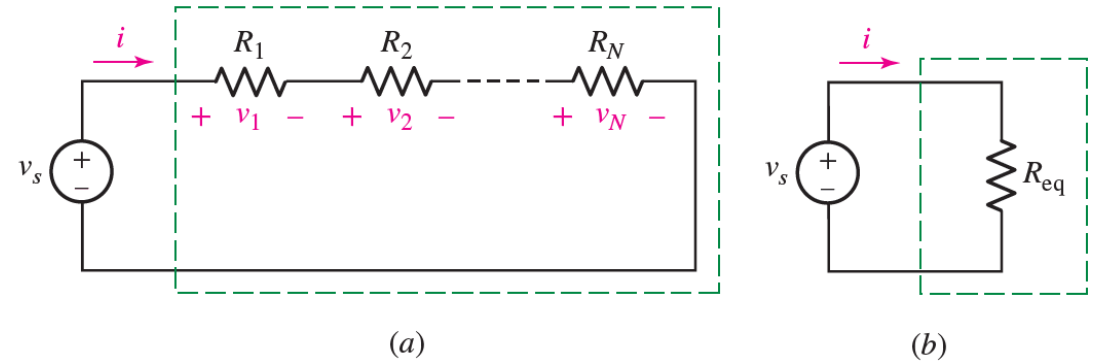

Example 1

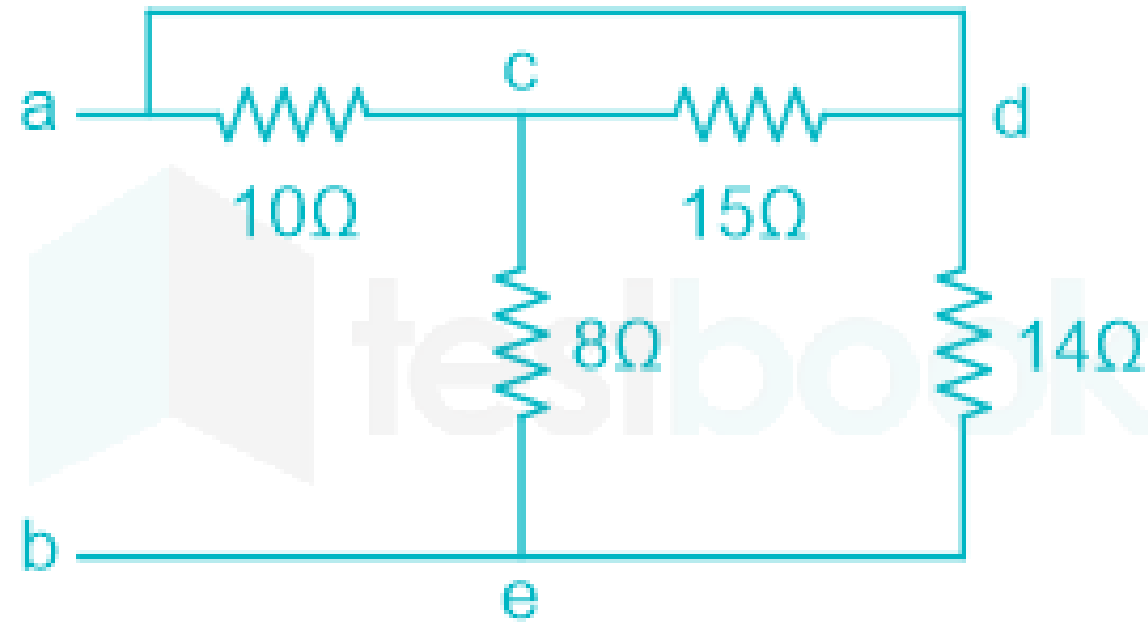

Example 2

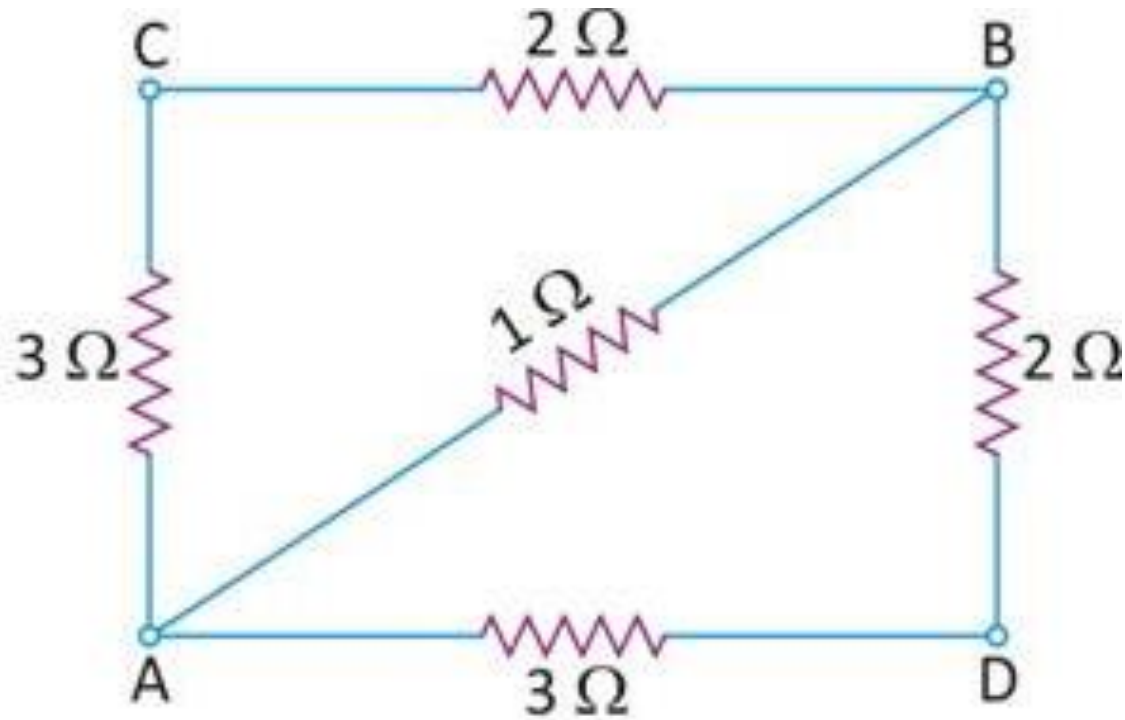

$$R_{AC} = 51/35 \, \Omega$$

$$R_{AB} = 25/35 \, \Omega$$

$$R_{BD} = 46/35 \, \Omega$$



$$R_{BC} = 46/35 \, \Omega$$

$$R_{AD} = 51/35 \, \Omega$$

$$R_{CD} = ?$$



Pi-Star transformation

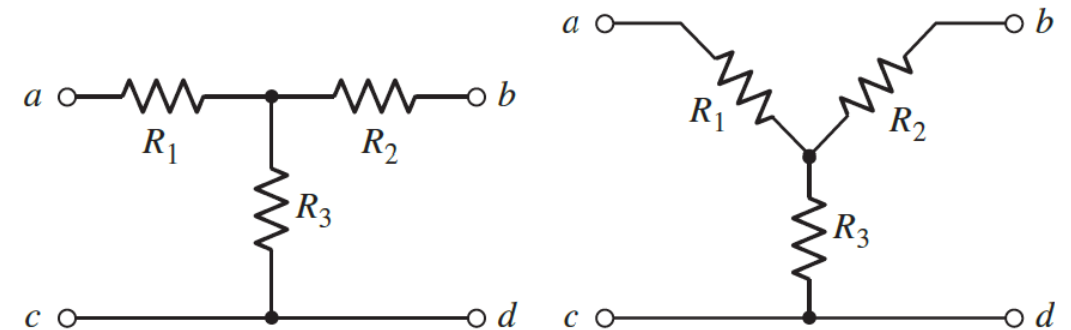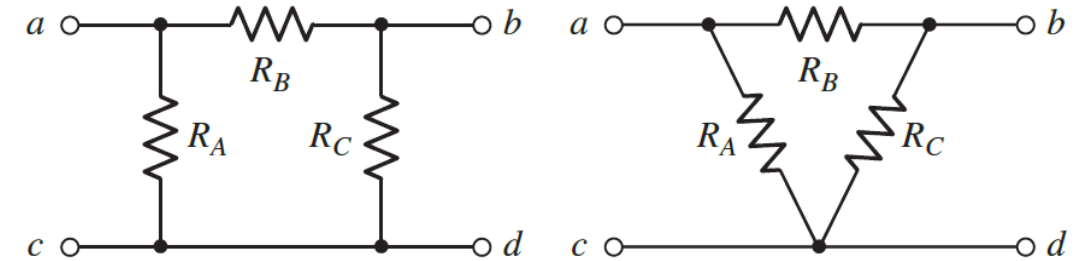- In some cases, the combination of series-parallel can be difficult to obtain
- In these cases, we need to perform some special operations and circuit equivalences
- One such equivalence is the Pi-Star equivalence, also known as Delta-Star or Delta-Wye transformation



Pi-Star transformation

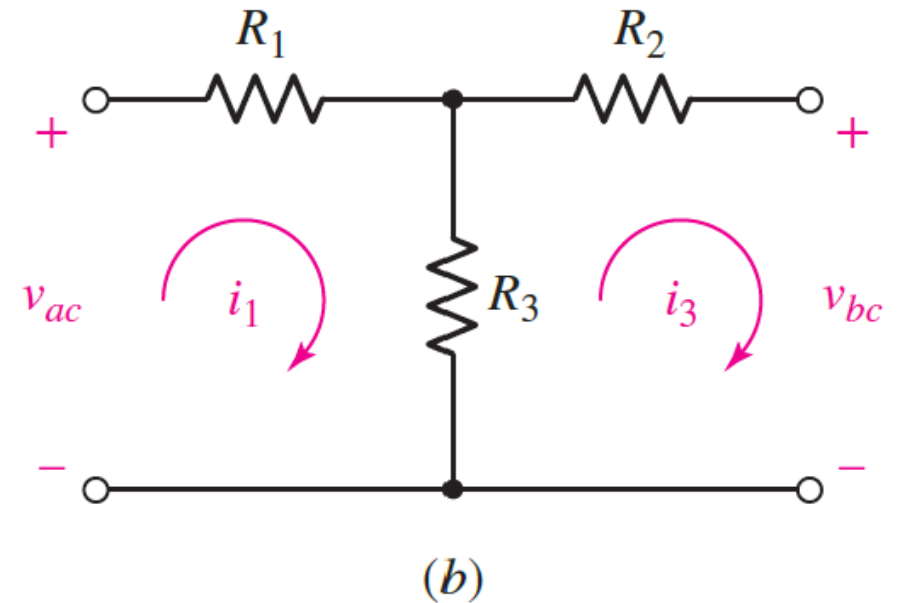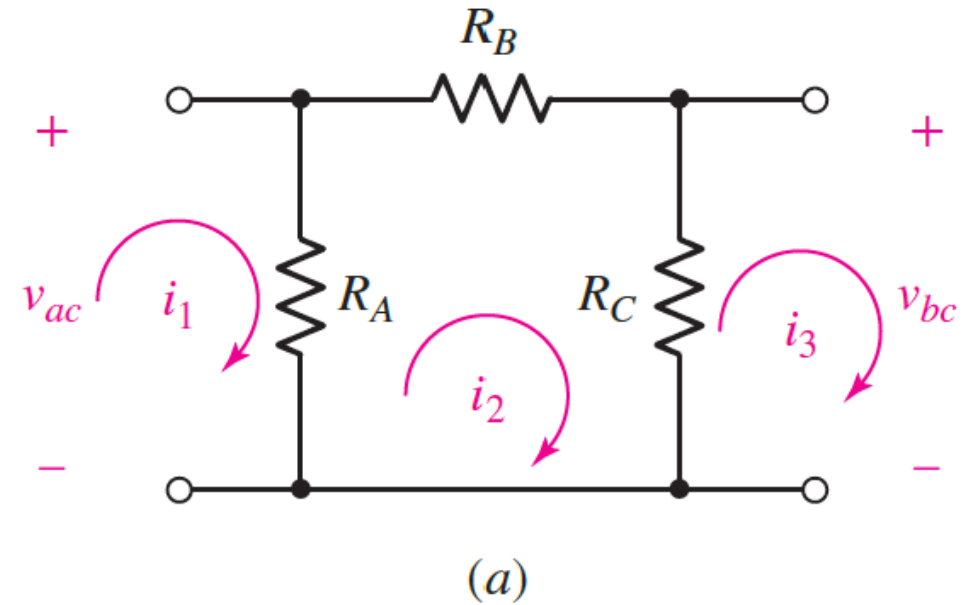- Say we want these two circuits to be “equivalent”
- Then, we need to make sure that voltages at the terminals and the currents entering/leaving the terminals are the same
- Thus, v_{ac} , v_{bc} , i_1 and i_3 should be same. i_2 is an internal current for the first circuit, and does not have a constraint



Pi-Star transformation

- For network (a):



$$\begin{aligned} R_A(i_1 - i_2) &= v_{ac} \\ -R_A(i_1 - i_2) + R_B i_2 + R_C(i_2 - i_3) &= 0 \\ R_C(i_2 - i_3) &= v_{bc} \end{aligned}$$

- For network (b):

$$\begin{aligned} R_1 i_1 + R_3(i_1 - i_3) &= v_{ac} \\ R_3(i_1 - i_3) - R_2 i_3 &= v_{bc} \end{aligned}$$

We can get i_2 as:
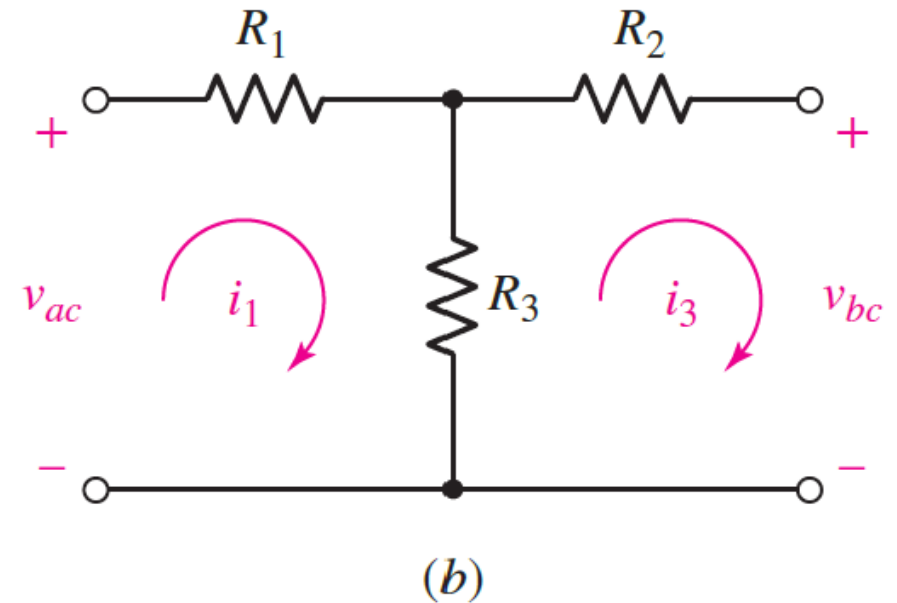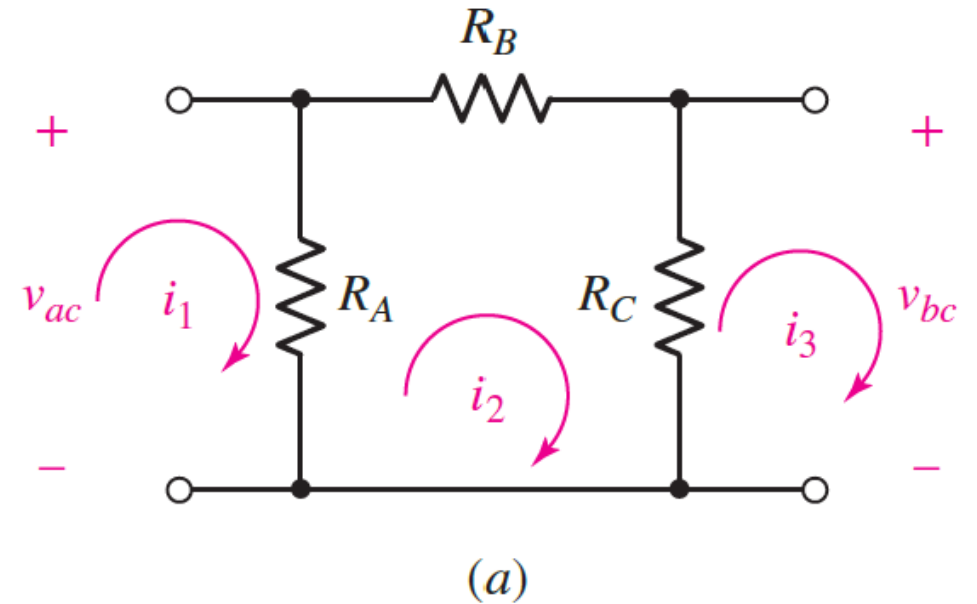
$$i_2 = \frac{R_A i_1 + R_C i_3}{R_A + R_B + R_C}$$



Pi-Star transformation

- For network (a):

$$R_A \left(i_1 - \frac{R_A i_1 + R_C i_3}{R_A + R_B + R_C} \right) = v_{ac}$$



$$\frac{R_A(R_B + R_C)i_1}{R_A + R_B + R_C} - \frac{R_A R_C i_3}{R_A + R_B + R_C} = v_{ac}$$

$$\frac{R_A R_C i_1}{R_A + R_B + R_C} - \frac{R_C(R_A + R_B)i_3}{R_A + R_B + R_C} = v_{bc}$$

- For network (b):

$$(R_1 + R_3)i_1 - R_3 i_3 = v_{ac}$$

$$R_3 i_1 - (R_2 + R_3)i_3 = v_{bc}$$

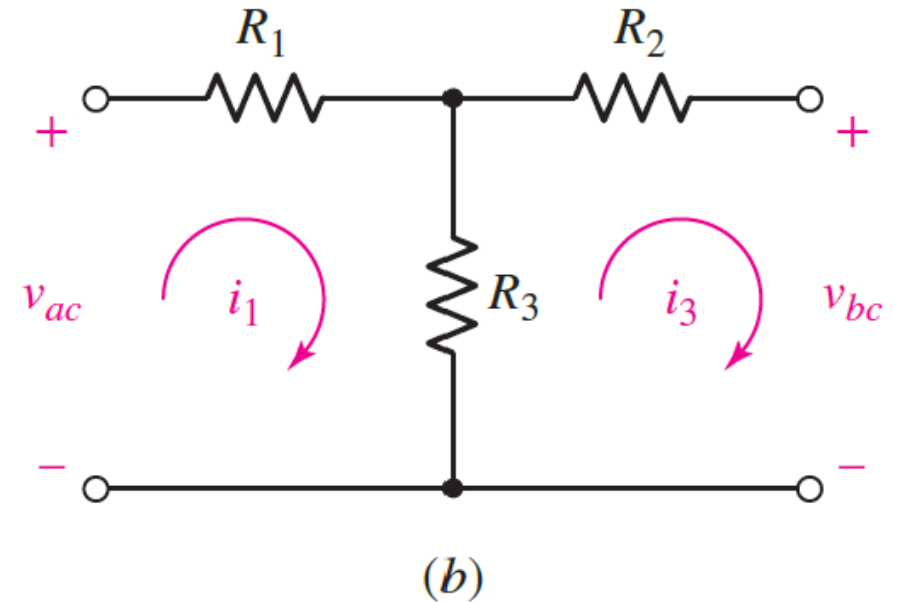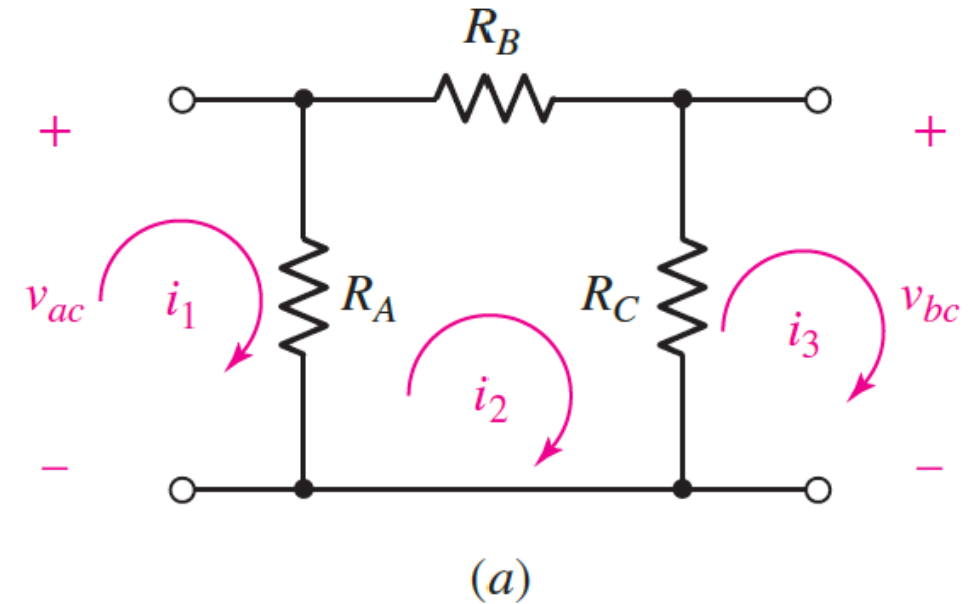

Pi-Star transformation

- For complete equivalence, the two sets of equations should have the same coefficients
- Thus,

$$R_3 = \frac{R_A R_C}{R_A + R_B + R_C}$$

- For the complete conversion:

$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$



$$R_2 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$R_3 = \frac{R_C R_A}{R_A + R_B + R_C}$$


$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

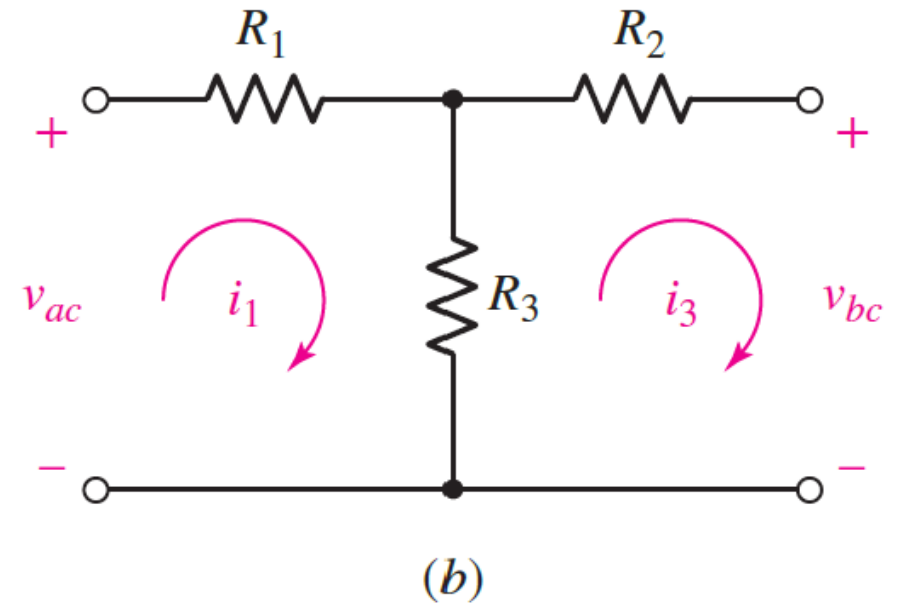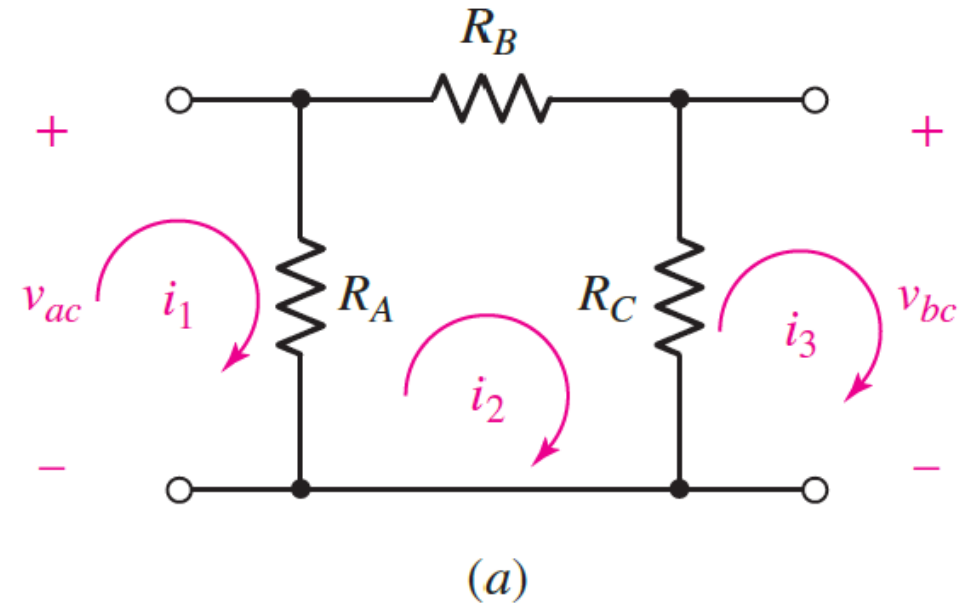

Example 2

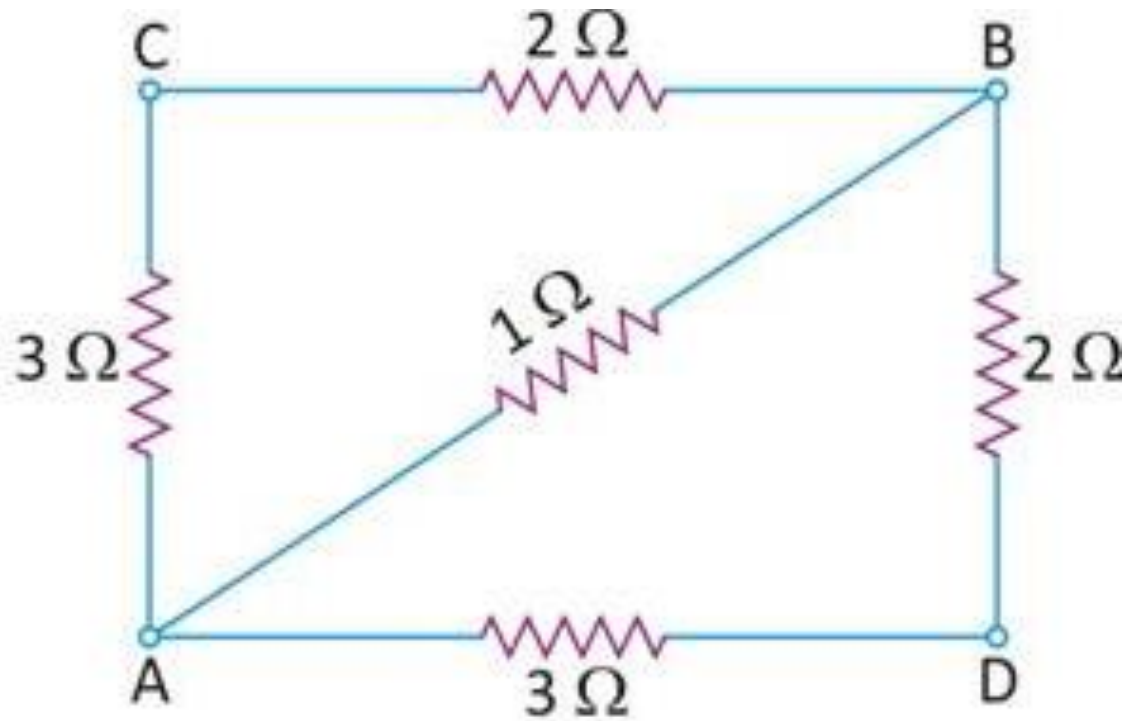

$$R_{AC} = 51/35\ \Omega$$

$$R_{AB} = 25/35\ \Omega$$

$$R_{BD} = 46/35\ \Omega$$

$$R_{BC} = 46/35\ \Omega$$

$$R_{AD} = 51/35\ \Omega$$

$$R_{CD} = ?$$